RTL-Assignment 1

December 20, 2022

		Sampath	Govardhan FWC22071
C	Contents		
1	Module Code		2
2	Test Bench Code		2
3	Timing diagram		2
4	Schematic diagram		2
5	Timing Report		2

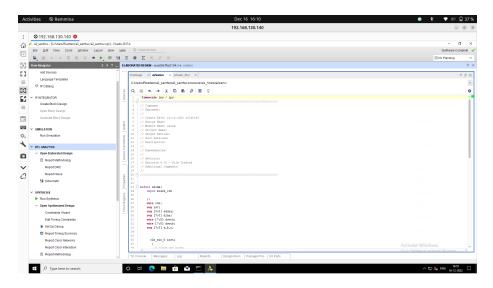


Figure 1: module code

1 Module Code

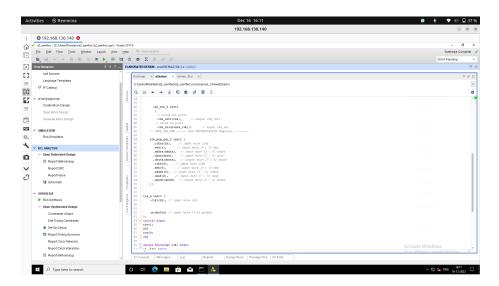


Figure 2: module code

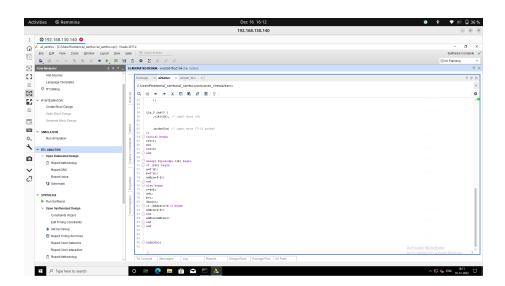


Figure 3: module code

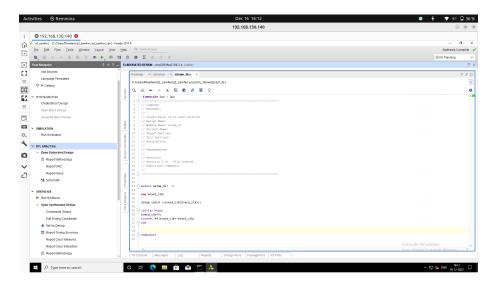


Figure 4: testbench code

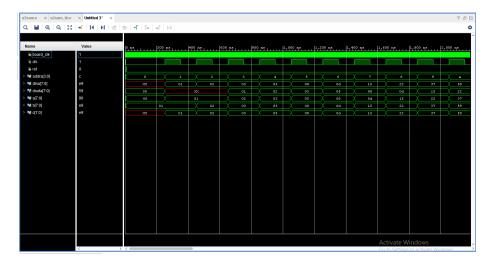


Figure 5: Timing diagram

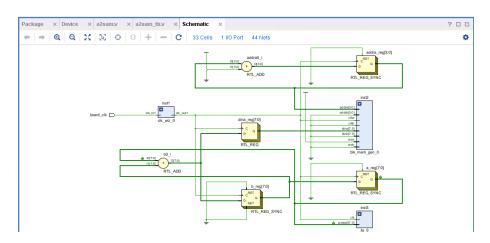


Figure 6: Schematic diagram

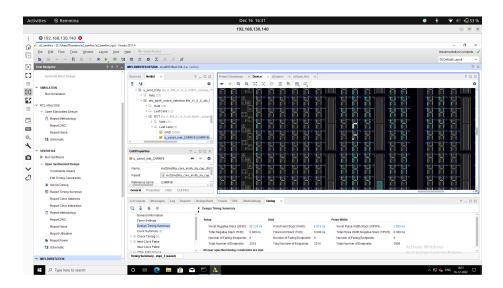


Figure 7: Timing Report